

Chapter 25 The Pipeline Analog to Digital Converter

The Pipeline ADC decides the bits of the output one by one. It first decides the most significant bit and then the second until the least significant bit is decided. Let us assume that the ADC outputs N bits, $b_{N-1}, b_{N-2}, \dots, b_0$. For any ADC, there will be an input V_{in} and a V_{ref} . The relationship between V_{in} , V_{ref} and the outputs bits are always as follows:

$$V_{in} = \sum_{i=0}^{N-1} b_i 2^i \frac{V_{ref}}{2^N} \quad (2.5-1)$$

Suppose $N=3$. Then we have the following formula:

$$\begin{aligned} V_{in} &= (b_2 2^2 + b_1 2^1 + b_0 2^0) \frac{V_{ref}}{2^3} \\ &= (b_2 \frac{V_{ref}}{2} + b_1 \frac{V_{ref}}{4} + b_0 \frac{V_{ref}}{8}) \end{aligned} \quad (2.5-2)$$

From Equation (2.5-2), we can easily see that if $V_{in} \geq \frac{V_{ref}}{2}$, b_2 must be set to be 1; otherwise, 0. This is how we can determine the value of b_2 .

Once b_2 is determined, we can determine b_1 as follows:

If $b_2=1$, we determine b_1 by comparing $V_{in} - \frac{V_{ref}}{2}$ with $\frac{V_{ref}}{4}$; otherwise, determine b_1 by comparing V_{in} with $\frac{V_{ref}}{4}$.

The above discussion can be generalized to N bits and the first subcircuit of the Pipeline ADC is illustrated in Fig. 25-1.

 


Fig. 25-1 The first stage of the Pipeline ADC

Let us try to understand the circuit in Fig. 25-1. Suppose the ADC has N bits as output. The input of V_{in} is first compared with $V_{ref}/2$. There are two cases:

Case 1: V_{in} is larger than $V_{ref}/2$, V_a will be high and $V(Q)$ will also be high. The high value of $V(Q)$ will cause the transmission gate to work and $V_{ref}/2$ will be transmitted to V_b . V_b will be $V_{ref}/2$ and b_N will be set to be 1. The connection of the inputs of the OP makes the OP to function as a subtractor. As can be seen, this output of the OP will be 2 times the difference of the inputs. Thus the output of the first stage is $2(V_{in} - V_{ref}/2)$.

Case 2: V_{in} is smaller than or equal to $V_{ref}/2$, V_a will be low and $V(QB)$ will be high. The high value of $V(QB)$ will cause the transmission gate not to function. Transistor $M1$ will be short circuited, V_b will be 0 and b_N will set to be 0. The output of the first stage is now $2(V_{in} - 0) = 2V_{in}$.

The output of the above circuit will be the input of the second stage of the Pipeline ADC. Therefore, we again have two cases;

Case 1: The output is $2(V_{in} - V_{ref}/2)$. In this case, we are going to compare $2(V_{in} - V_{ref}/2)$ with $V_{ref}/2$. If the result is larger than 0, it means $(V_{in} - V_{ref}/2) > V_{ref}/4$ and we then set b_{N-1} to be 1; otherwise, we set b_{N-1} to be 0.

Case 2: The output is $2(V_{in})$. In this case, we are going to compare $2(V_{in})$ with $V_{ref}/2$. If the result is larger than 0, it means $V_{in} > V_{ref}/4$ and we then set b_{N-1} to be 1; otherwise, we set b_{N-1} to be 0.

The Pipeline ADC will have N subcircuits as described in Fig. 25-1. These subcircuits will determine $b_N, b_{N-1}, \dots, b_0$ one by one. In Fig. 25-2, we show a Pipeline ADC with 3 output bits.

 


Fig. 25-2 A Pipeline ADC with three output bits

Let us give some examples. In all examples, $V_{ref}/2=0.8V$.

Example 25-1. $V_{in}=1.5V$

In this case, the circuits perform as below.

Stage 2: Since $V_{in2}=1.5V$ is larger than $V_{ref}/2=0.8V$, $Q2=high$ and the inputs of the subtractor are $V+=1.5V$ and $V-=0.8V$. $V_{out1}=2(1.5-0.8)V=1.4V$. This will be the input of Stage 1.

Stage 1: Since $V_{in1}=1.4V$ is larger than $V_{ref}/2=0.8V$, $Q1=high$ and the inputs of the subtractor are $V+=1.4V$ and $V-=0.8V$. $V_{out1}=2(1.4-0.8)V=1.2V$. This will be the input of Stage 0.

Stage 0: Since $V_{in1}=1.2V$ is larger than $V_{ref}/2=0.8V$, $Q0=high$.

For $V_{in}=1.5V$, $Q=(high, high, high)$. The ADC output is (111) which is correct.

Example 25-2 $V_{in}=0.3V$.

In this case, the circuits perform as below.

Stage 2: Since $V_{in2}=0.3V$ is smaller than $V_{ref}/2=0.8V$, $Q2=low$ and the inputs of the subtractor are $V+=0.3V$ and $V-=0V$. $V_{out1}=2(0.3-0)V=0.6V$. This will be the input of Stage 1.

Stage 1: Since $V_{in1}=0.6V$ is smaller than $V_{ref}/2=0.8V$, $Q1=low$ and the inputs of the subtractor are $V+=0.6V$ and $V-=0V$. $V_{out1}=2(0.6-0)V=1.2V$. This will be the input of Stage 0.

Stage 0: Since $V_{in0}=1.2V$ is larger than $V_{ref}/2=0.8V$, $Q0=high$.

For $V_{in}=0.3V$, $Q(low, low, high)$. The ADC output is (001) which is correct.

Example 25-3 $V_{in}=0.7V$

. In this case, the circuits perform as below.

Stage 2: Since $V_{in2}=0.7V$ is smaller than $V_{ref}/2=0.8V$, $Q2=low$ and the inputs of the subtractor are $V+=0.7V$ and $V-=0V$. $V_{out1}=2(0.7-0)V=1.4V$. This will be the input of Stage 1.

Stage 1: Since $V_{in1}=1.4V$ is larger than $V_{ref}/2=0.8V$, $Q1=high$ and the inputs of the subtractor are $V+=1.4V$ and $V-=0.8V$. $V_{out1}=2(1.4-0.8)V=1.2V$. This will be the input of Stage 0.

Stage 0: Since $V_{in0}=1.2V$ is larger than $V_{ref}/2=0.8V$, $Q0=high$.

For $V_{in}=0.3V$, $Q(low, high, high)$. The ADC output is (011) which is correct.

Section 25.1 The Rail to Rail Comparator Circuit

In the Pipeline ADC, the comparator may compare very small and very large numbers. Therefore we use the rail to rail comparator introduced in Chapter 3. The circuit is shown in Fig. 25.1-1.

 


Fig. 25.1-1 The comparator used in the Pipeline ADC.

Experiment 25.1-1 The Testing of the Rail to Rail Comparator

The program of this experiment is in Table 25.1-1 and the results are in Fig. 25.1-2. As can be seen, this comparator works correctly

Table 25.1-1 The program for Experiment 25.1-1

```
Rail_to_Rail_Comparator
.PROTECT
.OPTION POST
.lib "d:\model\tsmc\MIXED035\mm0355v.l" TT
.UNPROTECT
.op

M6      N1N322 N1N322 VSS VSS  NCH L=2U W=3U M=2
M3      N1N320 N1N320 VSS VSS  NCH L=2U W=3U M=2
M8      VVG I2U_S VDD VDD  PCH L=5U W=6U M=2
M1      N1N320 INN VVG VDD  PCH L=2U W=6U M=2
M2      N1N322 INP VVG VDD  PCH L=2U W=6U M=2
```

```

M7      I2U_S I2U_S VDD VDD   PCH L=5U W=6U M=2
M5      N1N365 N1N322 VSS VSS   NCH L=2U W=3U M=2
M4      N1N362 N1N320 VSS VSS   NCH L=2U W=3U M=2

M10     N1N362 INP N1N372 VSS   NCH L=2U W=3U M=2
M11     I2U I2U VSS VSS   NCH L=5U W=5U M=2
M12     N1N372 I2U VSS VSS   NCH L=5U W=5U M=2
M9      N1N365 INN N1N372 VSS   NCH L=2U W=3U M=2
M14     N1N362 N1N362 VDD VDD   PCH L=2U W=6U M=2
M13     N1N365 N1N365 VDD VDD   PCH L=2U W=6U M=2

M17     N1N431 N1N365 VDD VDD   PCH L=2U W=6U M=2
M18     VOUT N1N362 VDD VDD   PCH L=2U W=6U M=2
M15     N1N431 N1N431 VSS VSS   NCH L=2U W=3U M=2
M16     VOUT N1N431 VSS VSS   NCH L=2U W=3U M=2

```

```
vdd vdd gnd 1.6
```

```
vss vss gnd -1.6
```

```
v01 inn gnd 0.8
```

```
v02 inp gnd pwl(0 -1.5 0.5m 1.5 1m -1.5)
```

```
i01 i2u_s vss 2u
```

```
i02 vdd i2u 2u
```

```
.tran 0.1u 1m
```

```
.probe v(VOUT)
```

```
.END
```

 


Fig. 25.1-2 The results of Experiment 25.1-1

Section 25.2 The Connection of the Comparator with DFF and Non-overlapped Clock Generator

The Pipeline ADC needs a DFF and a non-overlapping clock generator. This DFF is connected to the output of a comparator. These circuits are shown in Fig. 25.2-1

 


Fig. 25.2-1 DFF and non-overlapped clock generator

Fig. 25.2-2 shows the connection of the comparator, the DFF and the clock.

 


Fig. 25.2-2 the comparator, the DFF and the clock

Experiment 25.2-1 The First Test of the DFF Circuit

The program of this experiment is in Table 25.2-1 and the results are shown in Fig. 25.2-3.

Table 25.2-1 The program for Experiment 25.2-1

Test of comparator and DFF

.PROTECT

.OPTION POST

.lib "d:\model\tsmc\MIXED035\mm0355v.l" TT

.UNPROTECT

.op

.subckt comparator INP INN VOUT I2U I2U_S VDD VSS

M6 N1N322 N1N322 VSS VSS NCH L=2U W=3U M=2

M3 N1N320 N1N320 VSS VSS NCH L=2U W=3U M=2

M8 VVG I2U_S VDD VDD PCH L=5U W=6U M=2

M1 N1N320 INN VVG VDD PCH L=2U W=6U M=2

M2 N1N322 INP VVG VDD PCH L=2U W=6U M=2

M7 I2U_S I2U_S VDD VDD PCH L=5U W=6U M=2

M5 N1N365 N1N322 VSS VSS NCH L=2U W=3U M=2

M4 N1N362 N1N320 VSS VSS NCH L=2U W=3U M=2

M10 N1N362 INP N1N372 VSS NCH L=2U W=3U M=2

M11 I2U I2U VSS VSS NCH L=5U W=5U M=2

M12 N1N372 I2U VSS VSS NCH L=5U W=5U M=2

M9 N1N365 INN N1N372 VSS NCH L=2U W=3U M=2

```

M14    N1N362 N1N362 VDD VDD  PCH L=2U W=6U M=2
M13    N1N365 N1N365 VDD VDD  PCH L=2U W=6U M=2

M17    N1N431 N1N365 VDD VDD  PCH L=2U W=6U M=2
M18    VOUT N1N362 VDD VDD  PCH L=2U W=6U M=2
M15    N1N431 N1N431 VSS VSS  NCH L=2U W=3U M=2
M16    VOUT N1N431 VSS VSS  NCH L=2U W=3U M=2
.ends

```

```

.subckt DFF CLK CLKB RESET D Q QB VDD VSS

```

```

MR1      RESETB RESET  VSS VSS NCH W=50u L=1u

```

```

MR2 RESETB  RESET  VDD VDD PCH W=50u L=1u

```

```

M1      D  CLKB    1  VSS NCH W=50u L=1u

```

```

MR3     1  RESETB  2  VSS NCH W=50u L=1u

```

```

MR4     2  RESET   VSS VSS NCH W=50u L=1u

```

```

MG11    3  2  VDD VDD PCH W=50u L=1u

```

```

MG12    3  2  VSS VSS NCH W=50u L=1u

```

```

MG13    4  3  VDD VDD PCH W=50u L=1u

```

```

MG14    4  3  VSS VSS NCH W=50u L=1u

```

```

M2      4  CLK  5  VSS NCH W=50u L=1u

```

```

MR5     5  RESETB  2  VSS NCH W=50u L=1u

```

```

M3      4  CLK  6  VSS NCH W=50u L=1u

```

```

MR6     6  RESETB  7  VSS NCH W=50u L=1u

```

```

MR7     7  RESET   VSS VSS NCH W=50u L=1u

```

```

MG21    9  7  VDD VDD PCH W=50u L=1u

```

```

MG22    9  7  VSS VSS NCH W=50u L=1u

```

```

MG23    Q  9  VDD VDD PCH W=50u L=1u

```

```

MG24    Q  9  VSS VSS NCH W=50u L=1u

```

```

M4      Q  CLKB    8  VSS NCH W=50u L=1u

```

```

MR8     7  RESETB  8  VSS NCH W=50u L=1u

```

```

MINV1  QB      Q      VSS VSS  NCH W=50u  L=1u
MINV2  QB      Q      VDD  VDD  PCH W=50u  L=1u
.ends

.subckt INV1 IN OUT VDD VSS
M1  OUT  IN      VDD  VDD  PCH  W=2U  L=1U
M2  OUT  IN      VSS  VSS  NCH  W=1U  L=1U
.ends

.subckt INV2 IN OUT VDD VSS
M1  OUT  IN      VDD  VDD  PCH  W=100U  L=2U
M2  OUT  IN      VSS  VSS  NCH  W=50U  L=2U
.ends

.subckt NOR A B OUT VDD VSS
M1  1    A      VDD  VDD  PCH  W=100U  L=2U
M2  OUT  B      1    VDD  PCH  W=100U  L=2U
M3  OUT  B      VSS  VSS  NCH  W=50U  L=2U
M4  OUT  A      VSS  VSS  NCH  W=50U  L=2U
.ends

.subckt NOVLP_CLK C C_Delayed CB_Delayed VDD VSS
X1 C CB VDD VSS INV1
X2 CB CBB VDD VSS INV2
X3 CBB CBBB VDD VSS INV1
X4 CBBB CBBBB VDD VSS INV2
R1 CBB C_Delayed 0
X7 C CBBBB CB_Delayed VDD VSS NOR
.ends

X1 vin vref a I2U I2U_S VDD VSS comparator
X2 CLK CLK_delayed CLKB_delayed VDD VSS NOVLP_CLK
X3 CLK_delayed CLKB_delayed RESET a Q QB VDD VSS DFF

vdd vdd 0 1.6
vss vss 0 -1.6

```

```

vref vref 0 0.8
vin vin 0 1.0

i01 i2u_s vss 2u
i02 vdd i2u 2u

Vclk CLK 0 pulse(-1.6v 1.6v 1.1us 0.01us 0.01us 0.13us 0.26us)
Vreset RESET 0 pulse(-1.6v 1.6v 0us 0.01us 0.01us 1us 20ms)

.tran 10ns 30us

.END

```

 


Fig. 25.2-3 The results of the Experiment 25.2-1

We can see that there are problems. Consider Fig. 25.2-1. V_a is obviously influenced by the signal CLKB which should not happen. This is due to the fact that the parasitic capacitor between the drain and gate of transistor M1 in D-flip-flop is too large. This causes the output of the comparator to be coupled by the clock signal CLKB.

To understand how the parasitic capacitance influences the circuit, we slightly modified the circuit by inserting a resistor with value 0 into the circuit as shown in Fig. 25.2-4.

 


Fig. 25.2-4 A slight modification of the circu

Experiment 25.2-2 A Testing of the Parasitic Capacitor

In this experiment, we test the circuit with the resistor R0 inserted. The program is Table 25.2-2 and the results are in Fig. 25.2-5.

Table 25.2-2 The program of Experiment 25.2-2

```
Test of comparator and DFF
.PROTECT
.OPTION POST
.lib "d:\model\tsmc\MIXED035\mm0355v.l" TT
.UNPROTECT
.op

.subckt comparator INP INN VOUT I2U I2U_S VDD VSS
M6      N1N322 N1N322 VSS VSS  NCH L=2U W=3U M=2
M3      N1N320 N1N320 VSS VSS  NCH L=2U W=3U M=2
M8      VVG I2U_S VDD VDD  PCH L=5U W=6U M=2
M1      N1N320 INN VVG VDD  PCH L=2U W=6U M=2
M2      N1N322 INP VVG VDD  PCH L=2U W=6U M=2
M7      I2U_S I2U_S VDD VDD  PCH L=5U W=6U M=2
M5      N1N365 N1N322 VSS VSS  NCH L=2U W=3U M=2
M4      N1N362 N1N320 VSS VSS  NCH L=2U W=3U M=2

M10     N1N362 INP N1N372 VSS  NCH L=2U W=3U M=2
```

```

M11    I2U I2U VSS VSS  NCH L=5U W=5U M=2
M12    N1N372 I2U VSS VSS  NCH L=5U W=5U M=2
M9     N1N365 INN N1N372 VSS  NCH L=2U W=3U M=2
M14    N1N362 N1N362 VDD VDD  PCH L=2U W=6U M=2
M13    N1N365 N1N365 VDD VDD  PCH L=2U W=6U M=2

M17    N1N431 N1N365 VDD VDD  PCH L=2U W=6U M=2
M18    VOUT N1N362 VDD VDD  PCH L=2U W=6U M=2
M15    N1N431 N1N431 VSS VSS  NCH L=2U W=3U M=2
M16    VOUT N1N431 VSS VSS  NCH L=2U W=3U M=2
.ends

.subckt DFF CLK CLKB RESET D Q QB VDD VSS
MR1     RESETB  RESET  VSS VSS NCH    W=50u  L=1u
MR2     RESETB RESET  VDD   VDD   PCHW=50u  L=1u

M1      D  CLKB   1  VSS NCH    W=50u  L=1u
MR3     1  RESETB 2  VSS NCH    W=50u  L=1u

MR4     2  RESET  VSS VSS NCH    W=50u  L=1u

MG11    3  2  VDD   VDD   PCHW=50u  L=1u
MG12    3  2  VSS VSS NCH    W=50u  L=1u
MG13    4  3  VDD   VDD   PCHW=50u  L=1u
MG14    4  3  VSS VSS NCH    W=50u  L=1u

M2      4  CLK    5  VSS NCH    W=50u  L=1u
MR5     5  RESETB 2  VSS NCH    W=50u  L=1u

M3      4  CLK    6  VSS NCH    W=50u  L=1u
MR6     6  RESETB 7  VSS NCH    W=50u  L=1u

MR7     7  RESET  VSS VSS NCH    W=50u  L=1u

MG21    9  7  VDD   VDD   PCHW=50u  L=1u
MG22    9  7  VSS VSS NCH    W=50u  L=1u
MG23    Q  9  VDD   VDD   PCHW=50u  L=1u
MG24    Q  9  VSS VSS NCH    W=50u  L=1u

```

```

M4      Q  CLKB  8  VSS NCH  W=50u  L=1u
MR8     7  RESETB 8  VSS NCH  W=50u  L=1u

MINV1   QB      Q      VSS  VSS NCH  W=50u  L=1u
MINV2   QB      Q      VDD  VDD    PCHW=50u  L=1u
.ends

.subckt INV1 IN OUT VDD VSS
M1      OUT  IN      VDD  VDD    PCH      W=2U    L=1U
M2      OUT  IN      VSS  VSS    NCH      W=1U    L=1U
.ends

.subckt INV2 IN OUT VDD VSS
M1      OUT  IN      VDD  VDD    PCH      W=100U   L=2U
M2      OUT  IN      VSS  VSS    NCH      W=50U    L=2U
.ends

.subckt NOR A B OUT VDD VSS
M1      1      A      VDD  VDD    PCH      W=100U   L=2U
M2      OUT    B      1      VDD    PCH      W=100U   L=2U
M3      OUT    B      VSS  VSS    NCH      W=50U    L=2U
M4      OUT    A      VSS  VSS    NCH      W=50U    L=2U
.ends

.subckt NOVLP_CLK C C_Delayed CB_Delayed VDD VSS
X1 C CB VDD VSS INV1
X2 CB CBB VDD VSS INV2
X3 CBB CBBB VDD VSS INV1
X4 CBBB CBBBB VDD VSS INV2
R1 CBB C_Delayed 0
X7 C CBBBB CB_Delayed VDD VSS NOR
.ends

X1 vin vref a I2U I2U_S VDD VSS comparator
X2 CLK CLK_delayed CLKB_delayed VDD VSS NOVLP_CLK
X3 CLK_delayed CLKB_delayed RESET a_tmp Q QB VDD VSS DFF

```

```

R0 a_tmp a 0

vdd vdd 0 1.6
vss vss 0 -1.6

vref vref 0 0.8
vin vin 0 1.0

i01 i2u_s vss 2u
i02 vdd i2u 2u

VclkCLK      0    pulse(-1.6v 1.6v  1.1us 0.01us 0.01us 0.13us 0.26us)
Vreset  RESET  0    pulse(-1.6v 1.6v  0us 0.01us 0.01us 1us 20ms)

.tran 10ns      30us
.probe I(R0) I(X1.M16) I(X1.M18)
.END

```

Fig. 25.2-5 shows that there is a current flowing through the resistor. This current is caused by the parasitic capacitor and should not exist. The existence of this current explains why the output of the comparator is influenced by the clock.

 


Fig. 25.2-5 The existence of current through the parasitic capacitance

Experiment 25.2-3 The Testing the Circuit Involving the Comparator and the DFF after Reducing the Gate Size of the M1 Transistor

To reduce the current as described above, we reduced the gate of the transistor M1. $V_{in} = 0.1V$. The program is in Table 25.2-2 and the results are in Fig. 25.2-6.

Table 25.2-23 The program for Experiment 25.2-2

```

Test of comparator and DFF
.PROTECT
.OPTION POST
.lib "d:\model\tsmc\MIXED035\mm0355v.l" TT
.UNPROTECT
.op

.subckt comparator INP INN VOUT I2U I2U_S VDD VSS
M6      N1N322 N1N322 VSS VSS  NCH L=2U W=3U M=2
M3      N1N320 N1N320 VSS VSS  NCH L=2U W=3U M=2
M8      VVG I2U_S VDD VDD  PCH L=5U W=6U M=2
M1      N1N320 INN VVG VDD  PCH L=2U W=6U M=2
M2      N1N322 INP VVG VDD  PCH L=2U W=6U M=2
M7      I2U_S I2U_S VDD VDD  PCH L=5U W=6U M=2
M5      N1N365 N1N322 VSS VSS  NCH L=2U W=3U M=2
M4      N1N362 N1N320 VSS VSS  NCH L=2U W=3U M=2

M10     N1N362 INP N1N372 VSS  NCH L=2U W=3U M=2
M11     I2U I2U VSS VSS  NCH L=5U W=5U M=2
M12     N1N372 I2U VSS VSS  NCH L=5U W=5U M=2
M9      N1N365 INN N1N372 VSS  NCH L=2U W=3U M=2
M14     N1N362 N1N362 VDD VDD  PCH L=2U W=6U M=2
M13     N1N365 N1N365 VDD VDD  PCH L=2U W=6U M=2

M17     N1N431 N1N365 VDD VDD  PCH L=2U W=6U M=2
M18     VOUT N1N362 VDD VDD  PCH L=2U W=6U M=2
M15     N1N431 N1N431 VSS VSS  NCH L=2U W=3U M=2
M16     VOUT N1N431 VSS VSS  NCH L=2U W=3U M=2
.ends

.subckt DFF CLK CLKB RESET D Q QB VDD VSS
MR1     RESETB RESET  VSS VSS NCH W=5u  L=1u
MR2     RESETB RESET  VDD VDD PCH W=5u  L=1u

```

```

M1      D   CLKB    1   VSS NCH W=5u   L=1u
MR3     1   RESETB  2   VSS NCH W=5u   L=1u

MR4     2   RESET   VSS VSS NCH W=5u   L=1u

MG11    3   2   VDD VDD PCH W=5u   L=1u
MG12    3   2   VSS VSS NCH W=5u   L=1u
MG13    4   3   VDD VDD PCH W=5u   L=1u
MG14    4   3   VSS VSS NCH W=5u   L=1u

M2      4   CLK  5   VSS NCH W=5u   L=1u
MR5     5   RESETB  2   VSS NCH W=5u   L=1u

M3      4   CLK  6   VSS NCH W=5u   L=1u
MR6     6   RESETB  7   VSS NCH W=5u   L=1u

MR7     7   RESET   VSS VSS NCH W=5u   L=1u

MG21    9   7   VDD VDD PCH W=5u   L=1u
MG22    9   7   VSS VSS NCH W=5u   L=1u
MG23    Q   9   VDD VDD PCH W=5u   L=1u
MG24    Q   9   VSS VSS NCH W=5u   L=1u

M4      Q   CLKB    8   VSS NCH W=5u   L=1u
MR8     7   RESETB  8   VSS NCH W=5u   L=1u

MINV1   QB      Q      VSS VSS NCH W=5u   L=1u
MINV2   QB      Q      VDD   VDD PCH W=5u   L=1u

```

```
.ends
```

```
.subckt INV1 IN OUT VDD VSS
```

```
M1      OUT    IN      VDD   VDD   PCH   W=2U   L=1U
```

```
M2      OUT    IN      VSS   VSS   NCH   W=1U   L=1U
```

```
.ends
```

```
.subckt INV2 IN OUT VDD VSS
```

```
M1      OUT    IN      VDD   VDD   PCH   W=10U  L=2U
```

```
M2      OUT    IN      VSS   VSS   NCH   W=5U   L=2U
```

```

.ends

.subckt NOR A B OUT VDD VSS
M1 1 A VDD VDD PCH W=10U L=2U
M2 OUT B 1 VDD PCH W=10U L=2U
M3 OUT B VSS VSS NCH W=5U L=2U
M4 OUT A VSS VSS NCH W=5U L=2U
.ends

.subckt NOVLP_CLK C C_Delayed CB_Delayed VDD VSS
X1 C CB VDD VSS INV1
X2 CB CBB VDD VSS INV2
X3 CBB CBBB VDD VSS INV1
X4 CBBB CBBB VDD VSS INV2
R1 CBB C_Delayed 0
X7 C CBBB CB_Delayed VDD VSS NOR
.ends

X1 vin vref a I2U I2U_S VDD VSS comparator
X2 CLK CLK_delayed CLKB_delayed VDD VSS NOVLP_CLK
X3 CLK_delayed CLKB_delayed RESET a_tmp Q QB VDD VSS DFF

R0 a_tmp a 0

vdd vdd 0 1.6
vss vss 0 -1.6

vref vref 0 0.8
vin vin 0 0.1

i01 i2u_s vss 2u
i02 vdd i2u 2u

Vclk CLK 0 pulse(-1.6v 1.6v 1.1us 0.01us 0.01us 0.13us 0.26us)
Vreset RESET 0 pulse(-1.6v 1.6v 0us 0.01us 0.01us 1us 20ms)

.tran 10ns 30us
.probe I(R0) I(X1.M16)

```

.END

 


Fig. 25.2-6 Results of Experiment 25.2-2 when $V_{in}=0.1V$

Note that the current through the resistor is greatly reduced. Because $V_{in}=0.1V$ is smaller than $V_{ref}/2=0.8V$, $Q=low$ and $QB=high$. The result is correct.

We then tested $V_{in}=1.0V$. The results are in Fig. 25.2-7.

 


Fig. 25.2-7 The results of Experiment 25.2-2 when $V_{in}=1.0V$

Because $V_{in}=1.0V$ is larger than $V_{ref}/2=0.8V$, $Q=high$ and $QB=low$. Besides, the currents have become very small

Section 25.3 The Testing of Comparator, Flip-Flop and the Transmission Gate

The transmission gate is shown in Fig. 25.3-1.

 


Fig. 25.3-1 The transmission gate circuit.

The circuit involving comparator, flip flop and transmission gate is shown in Fig. 25.3-2 .

 


Fig. 25.3-2 The circuit involving comparator, flip flop and transmission gate

Experiment 25.3-1 The Testing of Comparator , D Flip-Flop and Transmission Gate.

The program of this experiment is in Table 25.3-1. In the first test, $V_{in}=0.1V$. The results are in Fig. 25.3-3

Table 25.3-1 The program for the first test of Experiment 25.3-1

Test of comparator and DFF .PROTECT .OPTION POST
--

```

.lib "d:\model\tsmc\MIXED035\mm0355v.l" TT
.UNPROTECT
.op

.subckt comparator INP INN VOUT I2U I2U_S VDD VSS
M6      N1N322 N1N322 VSS VSS  NCH L=2U W=3U M=2
M3      N1N320 N1N320 VSS VSS  NCH L=2U W=3U M=2
M8      VVG I2U_S VDD VDD  PCH L=5U W=6U M=2
M1      N1N320 INN VVG VDD  PCH L=2U W=6U M=2
M2      N1N322 INP VVG VDD  PCH L=2U W=6U M=2
M7      I2U_S I2U_S VDD VDD  PCH L=5U W=6U M=2
M5      N1N365 N1N322 VSS VSS  NCH L=2U W=3U M=2
M4      N1N362 N1N320 VSS VSS  NCH L=2U W=3U M=2

M10     N1N362 INP N1N372 VSS  NCH L=2U W=3U M=2
M11     I2U I2U VSS VSS  NCH L=5U W=5U M=2
M12     N1N372 I2U VSS VSS  NCH L=5U W=5U M=2
M9      N1N365 INN N1N372 VSS  NCH L=2U W=3U M=2
M14     N1N362 N1N362 VDD VDD  PCH L=2U W=6U M=2
M13     N1N365 N1N365 VDD VDD  PCH L=2U W=6U M=2

M17     N1N431 N1N365 VDD VDD  PCH L=2U W=6U M=2
M18     VOUT N1N362 VDD VDD  PCH L=2U W=6U M=2
M15     N1N431 N1N431 VSS VSS  NCH L=2U W=3U M=2
M16     VOUT N1N431 VSS VSS  NCH L=2U W=3U M=2
.ends

.subckt DFF CLK CLKB RESET D Q QB VDD VSS
MR1     RESETB RESET  VSS VSS NCH W=5u  L=1u
MR2     RESETB RESET  VDD VDD PCH W=5u  L=1u

M1      D   CLKB    1   VSS NCH W=5u  L=1u
MR3     1   RESETB  2   VSS NCH W=5u  L=1u

MR4     2   RESET   VSS VSS NCH W=5u  L=1u

MG11    3   2   VDD VDD PCH W=5u  L=1u
MG12    3   2   VSS VSS NCH W=5u  L=1u

```

```

MG13  4  3  VDD VDD PCH W=5u  L=1u
MG14  4  3  VSS VSS NCH W=5u  L=1u

M2     4  CLK 5  VSS NCH W=5u  L=1u
MR5    5  RESETB 2  VSS NCH W=5u  L=1u

M3     4  CLK 6  VSS NCH W=5u  L=1u
MR6    6  RESETB 7  VSS NCH W=5u  L=1u

MR7    7  RESET  VSS VSS NCH W=5u  L=1u

MG21   9  7  VDD VDD PCH W=5u  L=1u
MG22   9  7  VSS VSS NCH W=5u  L=1u
MG23   Q  9  VDD VDD PCH W=5u  L=1u
MG24   Q  9  VSS VSS NCH W=5u  L=1u

M4     Q  CLKB  8  VSS NCH W=5u  L=1u
MR8    7  RESETB 8  VSS NCH W=5u  L=1u

MINV1  QB  Q  VSS VSS NCH W=5u  L=1u
MINV2  QB  Q  VDD  VDD PCH W=5u  L=1u
.ends

.subckt INV1 IN OUT VDD VSS
M1  OUT  IN  VDD  VDD  PCH  W=2U  L=1U
M2  OUT  IN  VSS  VSS  NCH  W=1U  L=1U
.ends

.subckt INV2 IN OUT VDD VSS
M1  OUT  IN  VDD  VDD  PCH  W=10U  L=2U
M2  OUT  IN  VSS  VSS  NCH  W=5U  L=2U
.ends

.subckt NOR A B OUT VDD VSS
M1  1  A  VDD  VDD  PCH  W=10U  L=2U
M2  OUT  B  1  VDD  PCH  W=10U  L=2U
M3  OUT  B  VSS  VSS  NCH  W=5U  L=2U
M4  OUT  A  VSS  VSS  NCH  W=5U  L=2U

```

```

.ends

.subckt NOVLP_CLK C C_Delayed CB_Delayed VDD VSS
X1 C CB VDD VSS INV1
X2 CB CBB VDD VSS INV2
X3 CBB CBBB VDD VSS INV1
X4 CBBB CBBB VDD VSS INV2
R1 CBB C_Delayed 0
X7 C CBBB CB_Delayed VDD VSS NOR
.ends

.subckt TG A B EN ENB VDD VSS
M1 A ENB B VDD PCH W=10U L=2U
M2 A EN B VSS NCH W=5U L=2U
.ends

X1 vin vref a I2U I2U_S VDD VSS comparator
X2 CLK CLK_delayed CLKB_delayed VDD VSS NOVLP_CLK
X3 CLK_delayed CLKB_delayed RESET a Q QB VDD VSS DFF
X4 Vref b Q QB VDD VSS TG

M1 b QB VSS VSS NCH W=5U L=2U

vdd vdd 0 1.6
vss vss 0 -1.6

vref vref 0 0.8
vin vin 0 0.1

i01 i2u_s vss 2u
i02 vdd i2u 2u

Vclk CLK 0 pulse(-1.6v 1.6v 1.1us 0.01us 0.01us 0.13us 0.26us)
Vreset RESET 0 pulse(-1.6v 1.6v 0us 0.01us 0.01us 1us 20ms)

.tran 10ns 30us

.END

```

Vin=0.1V

 


Fig. 25.3-3 The results of Experiment 25.3-1 for $V_{in}=0.1V$

Since $V_{in}=0.1V$, Q is negative, Vb is 0.

Fig. 25.3-4 shows the result of the testin when $V_{in}=1.0V$.


 


Fig. 25.3-4 The results of Experiment 25.3-1 for $V_{in}=1.0V$.

Since $V_{in}=1.0V$, Q is positive, Vb is $V_{ref}/2=0.8V$.

Section 25.4 The Subtractor Circuit

 The subtractor uses an OP, but this OP must be a rail to rail OP. We introduced this OP in Chapter 8 before. The circuit contains two parts. One part contains the circuit giving all of the voltage sources as shown in Fig. 25.4-1(a). The other is the rail to rail OP shown in Fig. 25.4-1(b).



(a)

 


Fig. 25.4-1 The rail to rail OP

Fig. 25.4-2 shows the subtractor and multiply by two circuit which we will use in our ADC circuit.

 


Fig. 25.4-2 The subtractor and multiply by two circuit

Experiment 25.4-1 The Testing of the subtractor and Multiply by Two Circuit

The program is in Table. 25.4-1. In the first test, $V1 = 0.8V$ and $V2 = 1.0V$. The results are in Fig. 25.4-3.

Table 25.4-1 The program of Experiment 25.4-1

```

Subtractor
.protect
.LIB "D:\model\tsmc\MIXED035\mm0355v.l" TT
.unprotect
.op
.options nomod post

VDD VDD    0    1.6V
VSS VSS    0    -1.6V

.subckt bias b1 b2 b3 b4 b5 b6 VDD VSS
R_bias    b7  VSS 0.5K

Mb1b1    b1  VSS VSS NCH W=10U L=1U
Mb2b8    b1  b7  VSS NCH W=10U L=1U

Mb3b1    b8  b9  VDD PCH W=20U L=1U
Mb5b9    b2  VDD VDD PCH W=20U L=1U

Mb4b8    b8  b2  VDD PCH W=20U L=1U
Mb6b2    b2  VDD VDD PCH W=20U L=1U

Mb8b10   b10 b4  VDD PCH W=20U L=1U
Mb9b4    b10 b11 VDD PCH W=20U L=1U
Mb10     b11 b11 VDD VDD PCH W=20U L=1U
Mb12     b6  b6  b12 VDD PCH W=20U L=1U
Mb13     b12 b12 VDD VDD PCH W=20U L=1U

Mb7b10   b1  VSS VSS NCH W=10U L=1U
Mb11     b6  b1  VSS VSS NCH W=10U L=1U

Mb15     b13 b13 b3  VSS NCH W=10U L=1U
Mb16     b3  b13 b14 VSS NCH W=10U L=1U
Mb17     b14 b14 VSS VSS NCH W=10U L=1U
Mb19     b5  b5  b15 VSS NCH W=10U L=1U
Mb20     b15 b15 VSS VSS NCH W=10U L=1U

```

```

Mb14    b13 b2  VDD VDD PCH W=20U  L=1U
Mb18    b5  b2  VDD VDD PCH W=20U  L=1U
.ends

```

```

.subckt opamp in+ in- out b1 b2 b3 b4 b5 b6 VDD VSS

```

```

M1 1 b1 VSS VSS NCH  W=10U  L=1U

```

```

M2 2 in+ 1 VSS NCH    W=10U  L=1U

```

```

M3 3 in- 1 VSS NCH W=10U  L=1U

```

```

M4 4 b2 VDD VDD PCH  W=20U  L=1U

```

```

M5 5 in+ 4 VDD PCH    W=20U  L=1U

```

```

M6 6 in- 4 VDD PCH    W=20U  L=1U

```

```

M7 3 7 VDD VDD PCH  W=20U  L=1U

```

```

M8 2 7 VDD VDD PCH  W=20U  L=1U

```

```

M9 7 b4 3 VDD PCH    W=20U  L=1U

```

```

M10 8 b4 2 VDD PCH   W=20U  L=1U

```

```

M11 9 b6 7 VDD PCH   W=20U  L=1U

```

```

M12 10 b6 8 VDD PCH  W=20U  L=1U

```

```

M13 7 b5 9 VSS NCH   W=10U  L=1U

```

```

M14 8 b5 10 VSS NCH  W=10U  L=1U

```

```

M15 9 b3 6 VSS NCH   W=10U  L=1U

```

```

M16 10 b3 5 VSS NCH  W=10U  L=1U

```

```

M17 6 9 VSS VSS NCH  W=10U  L=1U

```

```

M18 5 9 VSS VSS NCH  W=10U  L=1U

```

```

M19 out 8 VDD VDD PCH  W=20U  L=1U

```

```

M20 out 10 VSS VSS NCH W=10U  L=1U

```

```

.ends

```

```

X1 in+ in- out b1 b2 b3 b4 b5 b6 VDD VSS opamp

```

```

X2 b1 b2 b3 b4 b5 b6 VDD VSS bias

```

```

V1 V1 0 0.8V

```

```

V2 V2 0 1.0V

```

```

R1 V2 in+ 10K
R2 in+ 0 20K
R3 V1 in- 10K
R4 in- out 20K

.tran 10p 100n

.end

```

 


Fig. 25.4-3 The results of Experiment 25.4-1 for $V_1 = 0.8V$, $V_2 = 1.0V$

As can be seen, $V_{out} = (V_2 - V_1) * 2 = 0.4V$ which is correct.

We then test the case where $V_1=0V$ and $V_2=0.1V$. The results are in Fig. 25.4-4.

 


Fig. 25.4-4 The results of Experiment 25.4-1 for $V1 = 0V$, $V2 = 0.1V$

As can be seen, $V_{out} = (V2 - V1) * 2 = 0.2V$ which is correct.

Fig. 25.4-5 shows the result when $V1 = 0.8V$, $V2 = 1.6V$.

 


Fig. 25.4-5 The results of Experiment 25.4-1 for $V1 = 0.8V$, $V2 = 1.6V$

As can be seen, $V_{out} = (V2 - V1) * 2 = 1.6V$ which is correct.

Section 25.5 The Complete One Stage

In this section, we test the complete one stage circuit of the Pipeline ADC as shown in Fig. 25.5-1..


 


Fig. 25.5-1 The complete one stage circuit of the Pipeline ADC

 

Experiment 25.5-1 The Testing of the One Stage Pipeline ADC

The program of this experiment is in Table 25.5-1. The transmission gate and transistor M1 should be large enough to avoid voltage drop on the transmission gate and the transistor. For the first test, $V_{in}=1.0V$. The results are in Fig. 25.5-3.

Table 25.5-1 The program for Experiment 25.5-1

A stage of pipeline ADC			
.protect			
.LIB "D:\model\tsmc\MIXED035\mm0355v.l" TT			
.unprotect			
.op			
.options nomod post			
VDD	VDD	0	1.6V

VSS VSS 0 -1.6V

.subckt comparator INP INN VOUT I2U I2U_S VDD VSS

M6 N1N322 N1N322 VSS VSS NCH L=2U W=3U M=2

M3 N1N320 N1N320 VSS VSS NCH L=2U W=3U M=2

M8 VVG I2U_S VDD VDD PCH L=5U W=6U M=2

M1 N1N320 INN VVG VDD PCH L=2U W=6U M=2

M2 N1N322 INP VVG VDD PCH L=2U W=6U M=2

M7 I2U_S I2U_S VDD VDD PCH L=5U W=6U M=2

M5 N1N365 N1N322 VSS VSS NCH L=2U W=3U M=2

M4 N1N362 N1N320 VSS VSS NCH L=2U W=3U M=2

M10 N1N362 INP N1N372 VSS NCH L=2U W=3U M=2

M11 I2U I2U VSS VSS NCH L=5U W=5U M=2

M12 N1N372 I2U VSS VSS NCH L=5U W=5U M=2

M9 N1N365 INN N1N372 VSS NCH L=2U W=3U M=2

M14 N1N362 N1N362 VDD VDD PCH L=2U W=6U M=2

M13 N1N365 N1N365 VDD VDD PCH L=2U W=6U M=2

M17 N1N431 N1N365 VDD VDD PCH L=2U W=6U M=2

M18 VOUT N1N362 VDD VDD PCH L=2U W=6U M=2

M15 N1N431 N1N431 VSS VSS NCH L=2U W=3U M=2

M16 VOUT N1N431 VSS VSS NCH L=2U W=3U M=2

.ends

.subckt DFF CLK CLKB RESET D Q QB VDD VSS

MR1 RESETB RESET VSS VSS NCH W=5u L=1u

MR2 RESETB RESET VDD VDD PCH W=5u L=1u

M1 D CLKB 1 VSS NCH W=5u L=1u

MR3 1 RESETB 2 VSS NCH W=5u L=1u

MR4 2 RESET VSS VSS NCH W=5u L=1u

MG11 3 2 VDD VDD PCH W=5u L=1u

MG12 3 2 VSS VSS NCH W=5u L=1u

MG13 4 3 VDD VDD PCH W=5u L=1u

MG14 4 3 VSS VSS NCH W=5u L=1u

```

M2      4    CLK 5    VSS NCH W=5u    L=1u
MR5     5    RESETB 2    VSS NCH W=5u    L=1u

M3      4    CLK 6    VSS NCH W=5u    L=1u
MR6     6    RESETB 7    VSS NCH W=5u    L=1u

MR7     7    RESET    VSS VSS NCH W=5u    L=1u

MG21    9    7    VDD VDD PCH W=5u    L=1u
MG22    9    7    VSS VSS NCH W=5u    L=1u
MG23    Q    9    VDD VDD PCH W=5u    L=1u
MG24    Q    9    VSS VSS NCH W=5u    L=1u

M4      Q    CLKB    8    VSS NCH W=5u    L=1u
MR8     7    RESETB 8    VSS NCH W=5u    L=1u

MINV1   QB    Q      VSS VSS NCH W=5u    L=1u
MINV2   QB    Q      VDD    VDD PCH W=5u    L=1u

```

```
.ends
```

```
.subckt INV1 IN OUT VDD VSS
```

```

M1    OUT    IN      VDD    VDD    PCH    W=2U    L=1U
M2    OUT    IN      VSS    VSS    NCH    W=1U    L=1U

```

```
.ends
```

```
.subckt INV2 IN OUT VDD VSS
```

```

M1    OUT    IN      VDD    VDD    PCH    W=10U    L=2U
M2    OUT    IN      VSS    VSS    NCH    W=5U    L=2U

```

```
.ends
```

```
.subckt NOR A B OUT VDD VSS
```

```

M1    1      A      VDD    VDD    PCH    W=10U    L=2U
M2    OUT    B      1      VDD    PCH    W=10U    L=2U
M3    OUT    B      VSS    VSS    NCH    W=5U    L=2U
M4    OUT    A      VSS    VSS    NCH    W=5U    L=2U

```

```
.ends
```

```

.subckt NOVLP_CLK C C_Delayed CB_Delayed VDD VSS
X1 C CB VDD VSS INV1
X2 CB CBB VDD VSS INV2
X3 CBB CBBB VDD VSS INV1
X4 CBBB CBBB VDD VSS INV2
R1 CBB C_Delayed 0
X7 C CBBB CB_Delayed VDD VSS NOR
.ends

.subckt TG A B EN ENB VDD VSS
M1  A  ENB      B      VDD  PCH  W=100U  L=2U
M2  A  EN      B  VSS  NCH  W=50U  L=2U
.ends

.subckt bias b1 b2 b3 b4 b5 b6 VDD VSS
R_bias  b7  VSS 0.5K

Mb1b1  b1  VSS VSS NCH W=10U  L=1U
Mb2b8  b1  b7  VSS NCH W=10U  L=1U

Mb3b1  b8  b9  VDD PCH W=20U  L=1U
Mb5b9  b2  VDD VDD PCH W=20U  L=1U

Mb4b8  b8  b2  VDD PCH W=20U  L=1U
Mb6b2  b2  VDD VDD PCH W=20U  L=1U

Mb8b10 b10 b4  VDD PCH W=20U  L=1U
Mb9b4  b10 b11 VDD PCH W=20U  L=1U
Mb10   b11 b11 VDD VDD PCH W=20U  L=1U
Mb12   b6  b6  b12 VDD PCH W=20U  L=1U
Mb13   b12 b12 VDD VDD PCH W=20U  L=1U

Mb7b10 b1  VSS VSS NCH W=10U  L=1U
Mb11   b6  b1  VSS VSS NCH W=10U  L=1U

Mb15   b13 b13 b3  VSS NCH W=10U  L=1U
Mb16   b3  b13 b14 VSS NCH W=10U  L=1U
Mb17   b14 b14 VSS VSS NCH W=10U  L=1U

```

Mb19 b5 b5 b15 VSS NCH W=10U L=1U

Mb20 b15 b15 VSS VSS NCH W=10U L=1U

Mb14 b13 b2 VDD VDD PCH W=20U L=1U

Mb18 b5 b2 VDD VDD PCH W=20U L=1U

.ends

.subckt opamp in+ in- out b1 b2 b3 b4 b5 b6 VDD VSS

M1 1 b1 VSS VSS NCH W=10U L=1U

M2 2 in+ 1 VSS NCH W=10U L=1U

M3 3 in- 1 VSS NCH W=10U L=1U

M4 4 b2 VDD VDD PCH W=20U L=1U

M5 5 in+ 4 VDD PCH W=20U L=1U

M6 6 in- 4 VDD PCH W=20U L=1U

M7 3 7 VDD VDD PCH W=20U L=1U

M8 2 7 VDD VDD PCH W=20U L=1U

M9 7 b4 3 VDD PCH W=20U L=1U

M10 8 b4 2 VDD PCH W=20U L=1U

M11 9 b6 7 VDD PCH W=20U L=1U

M12 10 b6 8 VDD PCH W=20U L=1U

M13 7 b5 9 VSS NCH W=10U L=1U

M14 8 b5 10 VSS NCH W=10U L=1U

M15 9 b3 6 VSS NCH W=10U L=1U

M16 10 b3 5 VSS NCH W=10U L=1U

M17 6 9 VSS VSS NCH W=10U L=1U

M18 5 9 VSS VSS NCH W=10U L=1U

M19 out 8 VDD VDD PCH W=20U L=1U

M20 out 10 VSS VSS NCH W=10U L=1U

.ends

X1 vin vref a I2U I2U_S VDD VSS comparator

X2 CLK CLK_delayed CLKB_delayed VDD VSS NOVLP_CLK

X3 CLK_delayed CLKB_delayed RESET a Q QB VDD VSS DFF

```

X4 Vref b Q QB VDD VSS TG
X5 in+ in- out b1 b2 b3 b4 b5 b6 VDD VSS opamp
X6 b1 b2 b3 b4 b5 b6 VDD VSS bias

R1 vin in+ 20K
R2 in+ 0 40K
R3 b in- 20K
R4 in- out 40K

M1 b QB GND GND NCH W=50U L=2U

i01 i2u_s vss 2u
i02 vdd i2u 2u

vref vref 0 0.8
vin vin 0 0.4

Vclk CLK 0 pulse(-1.6v 1.6v 1.1us 0.01us 0.01us 0.13us 0.26us)
Vreset RESET 0 pulse(-1.6v 1.6v 0us 0.01us 0.01us 1us 20ms)

.tran 10ns 30us

.end

```

Vin = 1.0V


 


Fig. 25.5-3 The results of Experiment 25.5-1 when Vin=1.0V

Since $V_{in}=1.0V$ is larger than $V_{ref}/2=0.8V$, Q_0 = high and $V_{out} = (1.0 - 0.8) * 2 = 0.4V$.

 The results of $V_{in} = 0.4V$ is shown Fig. 25.5-4.



Since $V_{in}=1.0V$ is smaller than $V_{ref}/2=0.8V$, Q_0 = high and $V_{out} = (1.0 - 0.8) * 2 = 0.4V$.

Section 25.6. Two Stage Pipeline ADC

In this section, we assume that the output of the ADC needs two bits, For the Pipeline ADC, it therefore needs two stages as shown in Fig. 25.6-1

 


Fig. 25.6-1 A two stage Pipeline ADC.

Experiment 25.6-1 The Testing of the Two Stage Pipeline ADC.

The program is in Table 25.6-1. For the first test, $V_{in}=1.0V$. The results are in Fig. 25.6-2..

Table 25.6-1 The program for Experiment 25.6-1

```

Two stages
.protect
.LIB "D:\model\tsmc\MIXED035\mm0355v.l" TT
.unprotect
.op
.options nomod post

VDD VDD 0 1.6V
VSS VSS 0 -1.6V

.subckt comparator INP INN VOUT I2U I2U_S VDD VSS
M6 N1N322 N1N322 VSS VSS NCH L=2U W=3U M=2
M3 N1N320 N1N320 VSS VSS NCH L=2U W=3U M=2
M8 VVG I2U_S VDD VDD PCH L=5U W=6U M=2
M1 N1N320 INN VVG VDD PCH L=2U W=6U M=2
M2 N1N322 INP VVG VDD PCH L=2U W=6U M=2
M7 I2U_S I2U_S VDD VDD PCH L=5U W=6U M=2
M5 N1N365 N1N322 VSS VSS NCH L=2U W=3U M=2
M4 N1N362 N1N320 VSS VSS NCH L=2U W=3U M=2
  
```

```

M10    N1N362 INP N1N372 VSS  NCH L=2U W=3U M=2
M11    I2U I2U VSS VSS  NCH L=5U W=5U M=2
M12    N1N372 I2U VSS VSS  NCH L=5U W=5U M=2
M9     N1N365 INN N1N372 VSS  NCH L=2U W=3U M=2
M14    N1N362 N1N362 VDD VDD  PCH L=2U W=6U M=2
M13    N1N365 N1N365 VDD VDD  PCH L=2U W=6U M=2

M17    N1N431 N1N365 VDD VDD  PCH L=2U W=6U M=2
M18    VOUT N1N362 VDD VDD  PCH L=2U W=6U M=2
M15    N1N431 N1N431 VSS VSS  NCH L=2U W=3U M=2
M16    VOUT N1N431 VSS VSS  NCH L=2U W=3U M=2
.ends

```

```

.subckt DFF CLK CLKB RESET D Q QB VDD VSS

```

```

MR1      RESETB RESET  VSS VSS NCH W=5u  L=1u

```

```

MR2 RESETB  RESET  VDD VDD PCH W=5u  L=1u

```

```

M1      D  CLKB    1  VSS NCH W=5u  L=1u

```

```

MR3     1  RESETB  2  VSS NCH W=5u  L=1u

```

```

MR4     2  RESET  VSS VSS NCH W=5u  L=1u

```

```

MG11    3  2  VDD VDD PCH W=5u  L=1u

```

```

MG12    3  2  VSS VSS NCH W=5u  L=1u

```

```

MG13    4  3  VDD VDD PCH W=5u  L=1u

```

```

MG14    4  3  VSS VSS NCH W=5u  L=1u

```

```

M2      4  CLK 5  VSS NCH W=5u  L=1u

```

```

MR5     5  RESETB 2  VSS NCH W=5u  L=1u

```

```

M3      4  CLK 6  VSS NCH W=5u  L=1u

```

```

MR6     6  RESETB 7  VSS NCH W=5u  L=1u

```

```

MR7     7  RESET  VSS VSS NCH W=5u  L=1u

```

```

MG21    9  7  VDD VDD PCH W=5u  L=1u

```

```

MG22    9  7  VSS VSS NCH W=5u  L=1u

```

```

MG23  Q   9   VDD VDD PCH W=5u   L=1u
MG24  Q   9   VSS VSS NCH W=5u   L=1u

M4     Q   CLKB   8   VSS NCH W=5u   L=1u
MR8    7   RESETB  8   VSS NCH W=5u   L=1u

MINV1  QB     Q     VSS VSS NCH W=5u   L=1u
MINV2  QB     Q     VDD  VDD PCH W=5u   L=1u
.ends

.subckt INV1 IN OUT VDD VSS
M1     OUT   IN     VDD  VDD  PCH    W=2U   L=1U
M2     OUT   IN     VSS  VSS  NCH     W=1U   L=1U
.ends

.subckt INV2 IN OUT VDD VSS
M1     OUT   IN     VDD  VDD  PCH    W=10U  L=2U
M2     OUT   IN     VSS  VSS  NCH     W=5U   L=2U
.ends

.subckt NOR A B OUT VDD VSS
M1     1     A     VDD  VDD  PCH    W=10U  L=2U
M2     OUT   B     1    VDD  PCH    W=10U  L=2U
M3     OUT   B     VSS  VSS  NCH     W=5U   L=2U
M4     OUT   A     VSS  VSS  NCH     W=5U   L=2U
.ends

.subckt NOVLP_CLK C C_Delayed CB_Delayed VDD VSS
X1 C CB VDD VSS INV1
X2 CB CBB VDD VSS INV2
X3 CBB CBBB VDD VSS INV1
X4 CBBB CBBB VDD VSS INV2
R1 CBB C_Delayed 0
X7 C CBBB CB_Delayed VDD VSS NOR
.ends

.subckt TG A B EN ENB VDD VSS
M1     A     ENB     B     VDD  PCH    W=100U  L=2U

```

```
M2 A EN B VSS NCH W=50U L=2U
```

```
.ends
```

```
.subckt bias b1 b2 b3 b4 b5 b6 VDD VSS
```

```
R_bias b7 VSS 0.5K
```

```
Mb1b1 b1 VSS VSS NCH W=10U L=1U
```

```
Mb2b8 b1 b7 VSS NCH W=10U L=1U
```

```
Mb3b1 b8 b9 VDD PCH W=20U L=1U
```

```
Mb5b9 b2 VDD VDD PCH W=20U L=1U
```

```
Mb4b8 b8 b2 VDD PCH W=20U L=1U
```

```
Mb6b2 b2 VDD VDD PCH W=20U L=1U
```

```
Mb8b10 b10 b4 VDD PCH W=20U L=1U
```

```
Mb9b4 b10 b11 VDD PCH W=20U L=1U
```

```
Mb10 b11 b11 VDD VDD PCH W=20U L=1U
```

```
Mb12 b6 b6 b12 VDD PCH W=20U L=1U
```

```
Mb13 b12 b12 VDD VDD PCH W=20U L=1U
```

```
Mb7b10 b1 VSS VSS NCH W=10U L=1U
```

```
Mb11 b6 b1 VSS VSS NCH W=10U L=1U
```

```
Mb15 b13 b13 b3 VSS NCH W=10U L=1U
```

```
Mb16 b3 b13 b14 VSS NCH W=10U L=1U
```

```
Mb17 b14 b14 VSS VSS NCH W=10U L=1U
```

```
Mb19 b5 b5 b15 VSS NCH W=10U L=1U
```

```
Mb20 b15 b15 VSS VSS NCH W=10U L=1U
```

```
Mb14 b13 b2 VDD VDD PCH W=20U L=1U
```

```
Mb18 b5 b2 VDD VDD PCH W=20U L=1U
```

```
.ends
```

```
.subckt opamp in+ in- out b1 b2 b3 b4 b5 b6 VDD VSS
```

```
M1 1 b1 VSS VSS NCH W=10U L=1U
```

```
M2 2 in+ 1 VSS NCH W=10U L=1U
```

```
M3 3 in- 1 VSS NCH W=10U L=1U
```

```

M4 4 b2 VDD VDD PCH W=20U L=1U
M5 5 in+ 4 VDD PCH W=20U L=1U
M6 6 in- 4 VDD PCH W=20U L=1U

M7 3 7 VDD VDD PCH W=20U L=1U
M8 2 7 VDD VDD PCH W=20U L=1U
M9 7 b4 3 VDD PCH W=20U L=1U
M10 8 b4 2 VDD PCH W=20U L=1U

M11 9 b6 7 VDD PCH W=20U L=1U
M12 10 b6 8 VDD PCH W=20U L=1U
M13 7 b5 9 VSS NCH W=10U L=1U
M14 8 b5 10 VSS NCH W=10U L=1U

M15 9 b3 6 VSS NCH W=10U L=1U
M16 10 b3 5 VSS NCH W=10U L=1U
M17 6 9 VSS VSS NCH W=10U L=1U
M18 5 9 VSS VSS NCH W=10U L=1U

M19 out 8 VDD VDD PCH W=20U L=1U
M20 out 10 VSS VSS NCH W=10U L=1U
.ends

.subckt stage Vin Vref out CLK RESET Q VDD VSS
X1 vin vref a I2U I2U_S VDD VSS comparator
X2 CLK CLK_delayed CLKB_delayed VDD VSS NOVLP_CLK
X3 CLK_delayed CLKB_delayed RESET a Q QB VDD VSS DFF
X4 Vref b Q QB VDD VSS TG
X5 in+ in- out b1 b2 b3 b4 b5 b6 VDD VSS opamp
X6 b1 b2 b3 b4 b5 b6 VDD VSS bias

R1 vin in+ 20K
R2 in+ 0 40K
R3 b in- 20K
R4 in- out 40K

M1 b QB GND GND NCH W=50U L=2U

```

```

i01 i2u_s vss 2u
i02 vdd i2u 2u
.ends

X1 Vin Vref Vout1 CLK RESET Q1 VDD VSS stage
X2 Vout1 Vref Vout0 CLK RESET Q0 VDD VSS stage

vref vref 0 0.8
vin vin 0 0.6

Vclk CLK 0 pulse(-1.6v 1.6v 1.1us 0.01us 0.01us 0.13us 0.26us)
Vreset RESET 0 pulse(-1.6v 1.6v 0us 0.01us 0.01us 1us 20ms)

.tran 10ns 30us

.end

```

 


Fig. 25.6-2 The results of Experiment 25.6-1 when $V_{in}=1.0$

The Output = 10 which is correct.

Fig. 25.6-3 shows the results for $V_{in} = 1.4V$.

 


Fig. 25.6-3 The results of Experiment 25.6-3 when $V_{in}=1.4V$

The Output = 11 which is correct.

Fig. 25.6-4 shows the results for $V_{in} = 0.3V$.

 


Fig. 25.6-4 The results of Experiment 25.6-3 when $V_{in}=0.3V$

The Output = 00 which is correct.

Fig. 25.6-5 shows the results for $V_{in} = 0.6V$.

 


Fig. 25.6-5 The results of Experiment 25.6-3 when $V_{in}=0.6V$

The Output = 01 which is correct.

Section 25.7 Three Stage Pipeline ADC

In this section, we assume that the ADC has three bits as output.. Therefore we need three stages as shown in Fig. 25.7-1.

 


Fig. 25.7-1 The three stage Pipeline ADC

Experiment 25.7-1 The Testing of the Three Stage Pipeline ADC

The program is in Table 25.7-1. For the first test, $V_{in} = 1.5V$. The results are in Fig. 25.7-2.

Table 25.7-1 The program for Experiment 25.7-1

```
Two stages
.protect
.LIB "D:\model\tsmc\MIXED035\mm0355v.l" TT
.unprotect
.op
.options nomod post

VDD VDD 0 1.6V
VSS VSS 0 -1.6V

.subckt comparator INP INN VOUT I2U I2U_S VDD VSS
M6 N1N322 N1N322 VSS VSS NCH L=2U W=3U M=2
M3 N1N320 N1N320 VSS VSS NCH L=2U W=3U M=2
M8 VVG I2U_S VDD VDD PCH L=5U W=6U M=2
M1 N1N320 INN VVG VDD PCH L=2U W=6U M=2
M2 N1N322 INP VVG VDD PCH L=2U W=6U M=2
M7 I2U_S I2U_S VDD VDD PCH L=5U W=6U M=2
M5 N1N365 N1N322 VSS VSS NCH L=2U W=3U M=2
M4 N1N362 N1N320 VSS VSS NCH L=2U W=3U M=2

M10 N1N362 INP N1N372 VSS NCH L=2U W=3U M=2
```

```

M11    I2U I2U VSS VSS   NCH L=5U W=5U M=2
M12    N1N372 I2U VSS VSS   NCH L=5U W=5U M=2
M9     N1N365 INN N1N372 VSS   NCH L=2U W=3U M=2
M14    N1N362 N1N362 VDD VDD   PCH L=2U W=6U M=2
M13    N1N365 N1N365 VDD VDD   PCH L=2U W=6U M=2

M17    N1N431 N1N365 VDD VDD   PCH L=2U W=6U M=2
M18    VOUT N1N362 VDD VDD   PCH L=2U W=6U M=2
M15    N1N431 N1N431 VSS VSS   NCH L=2U W=3U M=2
M16    VOUT N1N431 VSS VSS   NCH L=2U W=3U M=2
.ends

```

```

.subckt DFF CLK CLKB RESET D Q QB VDD VSS

```

```

MR1     RESETB RESET   VSS VSS NCH W=5u   L=1u

```

```

MR2 RESETB  RESET   VDD VDD PCH W=5u   L=1u

```

```

M1      D    CLKB    1   VSS NCH W=5u   L=1u

```

```

MR3     1    RESETB  2   VSS NCH W=5u   L=1u

```

```

MR4     2     RESET   VSS VSS NCH W=5u   L=1u

```

```

MG11    3    2    VDD VDD PCH W=5u   L=1u

```

```

MG12    3    2    VSS VSS NCH W=5u   L=1u

```

```

MG13    4    3    VDD VDD PCH W=5u   L=1u

```

```

MG14    4    3    VSS VSS NCH W=5u   L=1u

```

```

M2      4    CLK  5   VSS NCH W=5u   L=1u

```

```

MR5     5    RESETB  2   VSS NCH W=5u   L=1u

```

```

M3      4    CLK  6   VSS NCH W=5u   L=1u

```

```

MR6     6    RESETB  7   VSS NCH W=5u   L=1u

```

```

MR7     7     RESET   VSS VSS NCH W=5u   L=1u

```

```

MG21    9    7    VDD VDD PCH W=5u   L=1u

```

```

MG22    9    7    VSS VSS NCH W=5u   L=1u

```

```

MG23    Q    9    VDD VDD PCH W=5u   L=1u

```

```

MG24    Q    9    VSS VSS NCH W=5u   L=1u

```

```

M4      Q   CLKB      8   VSS NCH W=5u   L=1u
MR8     7   RESETB    8   VSS NCH W=5u   L=1u

MINV1   QB      Q      VSS VSS NCH W=5u   L=1u
MINV2   QB      Q      VDD  VDD PCH W=5u   L=1u
.ends

.subckt INV1 IN OUT VDD VSS
M1      OUT    IN      VDD  VDD  PCH    W=2U    L=1U
M2      OUT    IN      VSS  VSS  NCH     W=1U    L=1U
.ends

.subckt INV2 IN OUT VDD VSS
M1      OUT    IN      VDD  VDD  PCH     W=10U   L=2U
M2      OUT    IN      VSS  VSS  NCH     W=5U    L=2U
.ends

.subckt NOR A B OUT VDD VSS
M1      1      A      VDD  VDD  PCH     W=10U   L=2U
M2      OUT    B      1    VDD  PCH     W=10U   L=2U
M3      OUT    B      VSS  VSS  NCH     W=5U    L=2U
M4      OUT    A      VSS  VSS  NCH     W=5U    L=2U
.ends

.subckt NOVLP_CLK C C_Delayed CB_Delayed VDD VSS
X1 C CB VDD VSS INV1
X2 CB CBB VDD VSS INV2
X3 CBB CBBB VDD VSS INV1
X4 CBBB CBBBB VDD VSS INV2
R1 CBB C_Delayed 0
X7 C CBBBB CB_Delayed VDD VSS NOR
.ends

.subckt TG A B EN ENB VDD VSS
M1      A      ENB      B      VDD  PCH    W=100U   L=2U
M2      A      EN      B      VSS  NCH    W=50U    L=2U
.ends

```

```

.subckt bias b1 b2 b3 b4 b5 b6 VDD VSS
R_bias    b7  VSS 0.5K

Mb1b1    b1  VSS VSS NCH W=10U  L=1U
Mb2b8    b1  b7  VSS NCH W=10U  L=1U

Mb3b1    b8  b9  VDD PCH W=20U  L=1U
Mb5b9    b2  VDD VDD PCH W=20U  L=1U

Mb4b8    b8  b2  VDD PCH W=20U  L=1U
Mb6b2    b2  VDD VDD PCH W=20U  L=1U

Mb8b10   b10 b4  VDD PCH W=20U  L=1U
Mb9b4    b10 b11 VDD PCH W=20U  L=1U
Mb10     b11 b11 VDD VDD PCH W=20U L=1U
Mb12     b6  b6  b12 VDD PCH W=20U L=1U
Mb13     b12 b12 VDD VDD PCH W=20U L=1U

Mb7b10   b1  VSS VSS NCH W=10U  L=1U
Mb11     b6  b1  VSS VSS NCH W=10U L=1U

Mb15     b13 b13 b3  VSS NCH W=10U L=1U
Mb16     b3  b13 b14 VSS NCH W=10U L=1U
Mb17     b14 b14 VSS VSS NCH W=10U L=1U
Mb19     b5  b5  b15 VSS NCH W=10U L=1U
Mb20     b15 b15 VSS VSS NCH W=10U L=1U

Mb14     b13 b2  VDD VDD PCH W=20U L=1U
Mb18     b5  b2  VDD VDD PCH W=20U L=1U
.ends

.subckt opamp in+ in- out b1 b2 b3 b4 b5 b6 VDD VSS
M1 1 b1 VSS VSS NCH W=10U L=1U
M2 2 in+ 1 VSS NCH W=10U L=1U
M3 3 in- 1 VSS NCH W=10U L=1U

M4 4 b2 VDD VDD PCH W=20U L=1U

```

```

M5 5 in+ 4 VDD PCH    W=20U  L=1U
M6 6 in- 4 VDD PCH    W=20U  L=1U

M7 3 7 VDD VDD PCH    W=20U  L=1U
M8 2 7 VDD VDD PCH    W=20U  L=1U
M9 7 b4 3 VDD PCH     W=20U  L=1U
M10 8 b4 2 VDD PCH    W=20U  L=1U

M11 9 b6 7 VDD PCH    W=20U  L=1U
M12 10 b6 8 VDD PCH   W=20U  L=1U
M13 7 b5 9 VSS NCH    W=10U  L=1U
M14 8 b5 10 VSS NCH   W=10U  L=1U

M15 9 b3 6 VSS NCH    W=10U  L=1U
M16 10 b3 5 VSS NCH   W=10U  L=1U
M17 6 9 VSS VSS NCH   W=10U  L=1U
M18 5 9 VSS VSS NCH   W=10U  L=1U

M19 out 8 VDD VDD PCH    W=20U  L=1U
M20 out 10 VSS VSS NCH   W=10U  L=1U
.ends

.subckt stage Vin Vref out CLK RESET Q VDD VSS
X1 vin vref a I2U I2U_S VDD VSS comparator
X2 CLK CLK_delayed CLKB_delayed VDD VSS NOVLP_CLK
X3 CLK_delayed CLKB_delayed RESET a Q QB VDD VSS DFF
X4 Vref b Q QB VDD VSS TG
X5 in+ in- out b1 b2 b3 b4 b5 b6 VDD VSS opamp
X6 b1 b2 b3 b4 b5 b6 VDD VSS bias

R1 vin in+ 20K
R2 in+ 0 40K
R3 b in- 20K
R4 in- out 40K

M1 b QB GND GND  NCH    W=50U    L=2U

i01 i2u_s vss 2u

```

```

i02 vdd i2u 2u
.ends

X1 Vin Vref Vout2 CLK RESET Q2 VDD VSS stage
X2 Vout2 Vref Vout1 CLK RESET Q1 VDD VSS stage
X3 Vout1 Vref Vout0 CLK RESET Q0 VDD VSS stage

vref vref 0 0.8
vin vin 0 1.1

Vclk CLK 0 pulse(-1.6v 1.6v 1.1us 0.01us 0.01us 0.13us 0.26us)
Vreset RESET 0 pulse(-1.6v 1.6v 0us 0.01us 0.01us 1us 20ms)

.tran 10ns 30us

.end

```

 


Fig. 25.7-2 The results of Experiment 25.7-1 when $V_{in}=1.5V$

The output = 111 which is correct.

Fig. 25.7-3 shows the result when $V_i=0.3V$.

 


Fig. 25.7-3 The results of Experiment 25.7-1 when $V_{in}=0.3V$

The output = 001 which is correct.

Fig. 25.7-4 shows the result when $V_i=1.1V$.

$V_{in} = 1.1V$

 


Fig. 25.7-4 The results of Experiment 25.7-1 when $V_{in}=1.1V$

The output = 101 which is correct.