

Chapter 37 Class G Power Amplifier

Class G power amplifier is similar to Class B power amplifier. Fig. 37-1 shows the schematic diagram of Class G power amplifier.

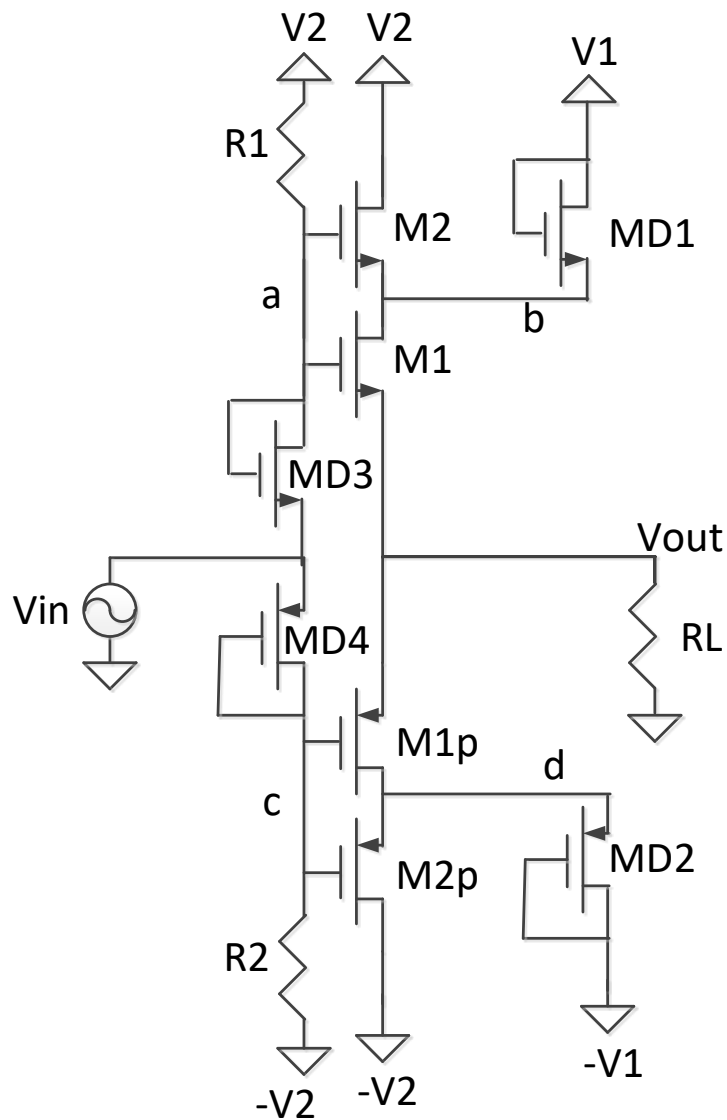


Fig. 37-1 A schematic diagram of Class G power amplifier

In the circuit shown in Fig. 37-1, the following needs to be noted.

- (1) There are two power supplies: V1 and V2. V1 is a small power supply while V2 is a larger power supply.
- (2) M2 and M1 are NMOS transistors while M1p and M2p are PMOS transistors.

- (3) MD1 to MD4 are all transistors connected as diodes.
- (4) The input V_{in} is a sinusoidal signal centered at 0.

The Class G power amplifier is designed to save energy. The circuit works as follows:

- (1) When V_{in} is positive, M1p and M2p are both cut off and M1 and M2 will be conducting.
- (2) If V_{in} is positive and small, V2 power supply will be cut off and only M1 will be conducting. Thus V1, which is a small power supply, is used in this case.
- (3) If V_{in} is positive and large, V1 power supply will be cut off and M2 and M1 will be conducting. Thus V2, which is a large power supply, is used in this case.
- (4) When V_{in} is negative, M1 and M2 are both cut off and M1p and M2p will be conducting.
- (5) If V_{in} is negative and small, -V2 will be cut off and only M1p will be conducting. Thus only -V1, which is a small power supply, is used in this case.
- (6) If V_{in} is negative and large, -V1 will be cut off and M2p and M1p will be conducting. Thus only -V2, which is a large power supply, is used in this case.

From the above discussion, we can see that Class G power amplifier is an improved version of Class B power amplifier. The amplitude of V_{in} can be quite large for Class G power amplifier. Therefore a large power supply needs to be used. It is important that this large power supply is used only when V_{in} is large in amplitude.

In the following, we will explain in detail how the circuit works. Consider Fig. 37-2.

 


Fig. 37-2 The four cases of V_{in}

We first note the following:

$$(1) \quad V_a = V_{in} + V_{th} . \quad (37-1)$$

$$(2) \quad V_b = V_1 - V_{th} . \quad (37-2)$$

Case 1 in Fig. 37-2.

In this case, V_{in} satisfies the following condition:

$$(V_1 - V_{th}) < V_{in} < V_2 . \quad (37.3)$$

$$V_{GS2} = V_a - V_b = V_{in} - V_1 + 2V_{th} = V_{in} - (V_1 - V_{th}) + V_{th} . \quad (37-4)$$

$$\text{Let } P = V_{in} - (V_1 - V_{th}) \quad (37-5)$$

Since we assume that V_{in} is larger than $V_1 - V_{th}$, P is positive. From Equation (37-4), we have

$$V_{GS2} = P + V_{th} > V_{th} \quad (37-6)$$

and M_2 will conduct in this case. That is, M_2 conducts when

$$V_{in} > V_1 - V_{th} . \quad (37-7)$$

As soon as M2 conducts, V_b will rise, MD1 will be reversely biased and V1 will be blocked. That is, only V2 is used in this case. Note that since M2 conducts, M1 must also conduct. We now discuss why current can flow in M1.

The condition for M1 to conduct is as follows:

$$V_{GS1} = V_a - V_{out} = V_{in} + V_{th} - V_{out} > V_{th} \quad (37-8)$$

Thus we must make sure that V_{in} is larger than or equal to V_{out} . This can be achieved by carefully adjusting parameters of the circuit.

We may summarize Case 1 as follows:

- (1) V1 is blocked and V2 is used.
- (2) M2 and M1 both conduct.
- (3) Current flows from V2 through M2 and M1 to RL

Case 2 in Fig. 37-2.

In this case, V_{in} satisfies the following condition:

$$0 < V_{in} < (V_1 - V_{th}). \quad (37-9)$$

It can be easily seen that under such condition, we will have:

$$V_{GS2} = P + V_{th} < V_{th}, \quad (37-10)$$

because P is negative. Thus M2 will be cut off, V2 will not be used.

The discussion about M1 in Case 1 is still valid in Case 2. Thus only M1 conducts and V1 is used. We therefore may summarize Case 2 as follows:

- (1) V2 is cut off and V1 is used.
- (2) Only M1 conducts.
- (3) Current flows from V1 through M1 to RL.

As for Cases 3 to 4, note that in these two cases, V_{in} is below 0. Since the circuit

in Fig. 37-1 is symmetrical, by slightly modifying the discussion of Cases 1 to 2, we can show that $M2p$ will conduct only when the absolute value of the amplitude of V_{in} is large.

In the following section, we will conduct some experiments of the Class G power amplifier circuit shown in Fig. 37-1.

Section 37.1 Testing of the Class G Power Amplifier

Circuit

Experiment 37.1-1 The First Test of the Class G Power Amplifier Circuit Shown in Fig. 37-1.

In this test, the circuit is the one shown in Fig. 37-1. The program is in Table 37.1-1 and the results are in Fig. 37.1-1. Some important parameters are shown below.

R1=R2=5K

V2=5V

V1=3V

All transistors are power transistors

Vth=2V for all transistors

RL=50

Vin amplitude=1.5V, DC=0, frequency=3KHz

Table 37.1-1 The program for Experiment 37.1-1

```
amplifier
.protect
.lib "C:\model\tsmc\MIXED035\mm0355v.l" TT
.unprotect
.op
.options nomod post

V1 V1 0 3v
V2 V2 0 5v
V1p V1p 0 -3v
V2p V2p 0 -5v

R1 V2 a 5K
R2 V2p c 5K

M1 b a OUT V2p M2N6802 W=2u L=2u
M2 V2 a b V2p M2N6802 W=4u L=2u
```

```

M1p  d  c  OUT V2  M2N6804  W=2u L=2u
M2p  V2p c  d  V2  M2N6804  W=4u L=2u

MD1  V1  V1  b  V2p M2N6802  W=4u L=2u
MD2  V1p V1p d  V2  M2N6804  W=4u L=2u
MD3  a  a  IN  V2p M2N6802  W=2u L=2u
MD4  c  c  IN  V2  M2N6804  W=2u L=2u

RL  OUT 0  50

.model M2N6802  NMOS(Level=3 Gamma=0 Delta=0 Eta=0 Theta=0 Kappa=0
Vmax=0 Xj=0
+      Tox=100n Uo=600 Phi=.6 Rs=.1084 Kp=20.88  Vto=2 NSUB=1E15
+      Rd=1.163  Cbd=732p Pb=.8 Mj=.5 Fc=.5 Cgso=1.725n
+      Cgdo=136.7p  Is=1.823p N=1 Tt=2060n)

.model M2N6804  PMOS(Level=3 Gamma=0 Delta=0 Eta=0 Theta=0 Kappa=0
Vmax=0 Xj=0
+      Tox=100n Uo=300 Phi=.6 Rs=.153 Kp=10.46 Vto=-2 NSUB=1E15
+      Rd=66.52m  Cbd=1.281n Pb=.8 Mj=.5 Fc=.5 Cgso=1.798n
+      Cgdo=134.9p  Is=5.477p N=3 Tt=295n)

Vin  IN  0  sin(0V 1.5V 3K)

.tran 0.1us 0.6ms
.probe TRAN I(M1) I(M2) I(M1p) I(M2p) power=PAR('V(OUT)*I(RL)')

.end

```

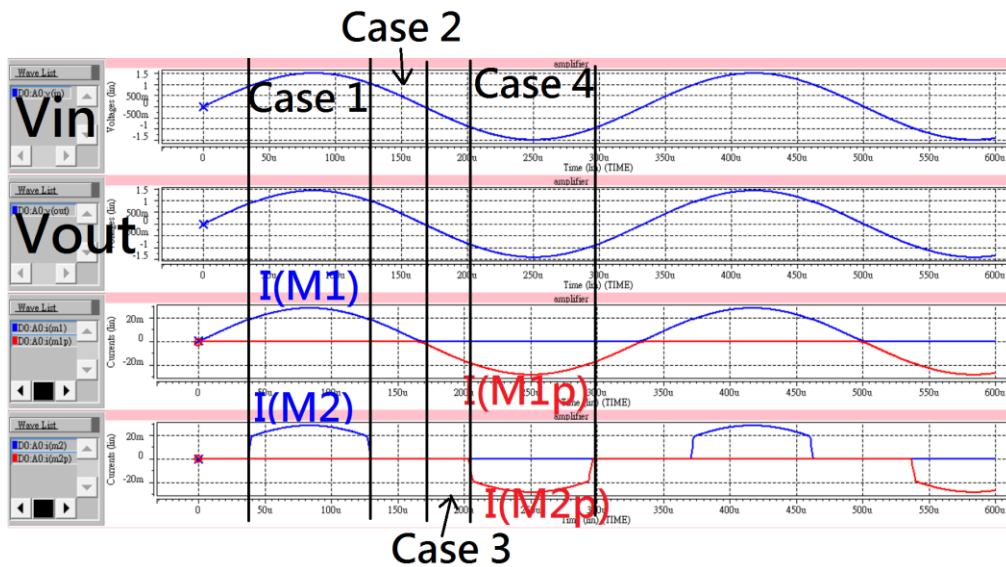


Fig. 37.1-1 The results of Experiment 37.1-1

From Fig. 37.1-1, we can see the following:

- (1) Only M1 and M2 conduct when V_{in} is positive.
- (2) Only M1p and M2P conduct when V_{in} is negative.
- (3) M2 and M2p conduct only when the amplitude of V_{in} assumes large value.
- (4) $V_1=3$ and $V_{th}=2$. $V_1-V_{th}=3-2=1$. M2 is turned on when V_{in} is larger than 1V which is predicted by Equation (37-7).
- (5) V_{out} amplitude=1.5V, DC=0, frequency=3KHz

In summary, the experimental results of Experiment 37.1-1 show that the circuit in Fig. 37-1 works as a Class G power amplifier and validates the discussion about the circuit at the beginning of this chapter.

Section 37.2 More Experiments

Class G power amplifiers are often used in audio systems. Therefore we like to know whether the amplifier discussed in this chapter can handle signal with frequency up to 100KHz.

Experiment 37.2-1 Increasing Input Frequency from 3kHz to 100Kz

In this experiment, we increase the input frequency from 3KHz to 100KHz. The program is in Table 37.2-1 and the results are in Fig. 37.2-1. As can be seen, the circuit works well for this frequency.

Table 37.2-1 The program for Experiment 27.2-1

```
amplifier
.protect
.lib "C:\model\tsmc\MIXED035\mm0355v.l" TT
.unprotect
.op
.options nomod post

V1 V1 0 3v
V2 V2 0 5v
V1p V1p 0 -3v
V2p V2p 0 -5v

R1 V2 a 5K
R2 V2p c 5K

M1 b a OUT V2p M2N6802 W=2u L=2u
M2 V2 a b V2p M2N6802 W=4u L=2u
M1p d c OUT V2 M2N6804 W=2u L=2u
M2p V2p c d V2 M2N6804 W=4u L=2u

MD1 V1 V1 b V2p M2N6802 W=4u L=2u
MD2 V1p V1p d V2 M2N6804 W=4u L=2u
MD3 a a IN V2p M2N6802 W=2u L=2u
MD4 c c IN V2 M2N6804 W=2u L=2u
```

```
RL OUT 0 50
```

```
.model M2N6802 NMOS(Level=3 Gamma=0 Delta=0 Eta=0 Theta=0 Kappa=0  
Vmax=0 Xj=0
```

```
+ Tox=100n Uo=600 Phi=.6 Rs=.1084 Kp=20.88 Vto=2 NSUB=1E15
```

```
+ Rd=1.163 Cbd=732p Pb=.8 Mj=.5 Fc=.5 Cgso=1.725n
```

```
+ Cgdo=136.7p Is=1.823p N=1 Tt=2060n)
```

```
.model M2N6804 PMOS(Level=3 Gamma=0 Delta=0 Eta=0 Theta=0 Kappa=0
```

```
Vmax=0 Xj=0
```

```
+ Tox=100n Uo=300 Phi=.6 Rs=.153 Kp=10.46 Vto=-2 NSUB=1E15
```

```
+ Rd=66.52m Cbd=1.281n Pb=.8 Mj=.5 Fc=.5 Cgso=1.798n
```

```
+ Cgdo=134.9p Is=5.477p N=3 Tt=295n)
```

```
Vin IN 0 sin(0V 1.5V 100K)
```

```
.tran 0.1us 0.6ms
```

```
.probe TRAN I(M1) I(M2) I(M1p) I(M2p) power=PAR('V(OUT)*I(RL)') V(a,b) V(c,d)
```

```
V(a,OUT) V(c,OUT)
```

```
.end
```

 


Fig. 37.2-1 The results of Experiment 37.2-1

In the previous experiments, we used power transistors which allow large current

to flow. In the following experiment, we will use ordinary transistors to see whether the circuit will work.

Experiment 37.2-2 Using Ordinary Transistors

In this experiment, we used ordinary transistors. In order to allow large current to flow, we actually used 60 transistors in parallel. The program is in Table 37.2-2 and the results are in Fig. 37.2-2. As can be seen, the amplitude of V_{out} decreased from 1.5V to 0.3V. Besides, V_{out} is distorted. Thus, ordinary transistors cannot be used for Class G power amplifier.

Table 37.2-2 The program for Experiment 37.2-2

```

amplifier
.protect
.lib "C:\model\tsmc\MIXED035\mm0355v.l" TT
.unprotect
.op
.options nomod post

V1 V1 0 3v
V2 V2 0 5v
V1p V1p 0 -3v
V2p V2p 0 -5v

R1 V2 a 5K
R2 V2p c 5K

M1 b a OUT V2p NCH W=2u L=2u m=60
M2 V2 a b V2p NCH W=4u L=2u m=60
M1p d c OUT V2 PCH W=2u L=2u m=60
M2p V2p c d V2 PCH W=4u L=2u m=60

MD1 V1 V1 b V2p NCH W=4u L=2u m=60
MD2 V1p V1p d V2 PCH W=4u L=2u m=60
MD3 a a IN V2p NCH W=2u L=2u m=60
MD4 c c IN V2 PCH W=2u L=2u m=60

RL OUT 0 50

```

```

.model M2N6802 NMOS(Level=3 Gamma=0 Delta=0 Eta=0 Theta=0 Kappa=0
Vmax=0 Xj=0
+      Tox=100n Uo=600 Phi=.6 Rs=.1084 Kp=20.88 Vto=2 NSUB=1E15
+      Rd=1.163 Cbd=732p Pb=.8 Mj=.5 Fc=.5 Cgso=1.725n
+      Cgdo=136.7p Is=1.823p N=1 Tt=2060n)

.model M2N6804 PMOS(Level=3 Gamma=0 Delta=0 Eta=0 Theta=0 Kappa=0
Vmax=0 Xj=0
+      Tox=100n Uo=300 Phi=.6 Rs=.153 Kp=10.46 Vto=-2 NSUB=1E15
+      Rd=66.52m Cbd=1.281n Pb=.8 Mj=.5 Fc=.5 Cgso=1.798n
+      Cgdo=134.9p Is=5.477p N=3 Tt=295n)

Vin IN 0 sin(0V 1.5V 100K)

.tran 0.1us 0.6ms
.probe TRAN I(M1) I(M2) I(M1p) I(M2p) power=PAR('V(OUT)*I(RL)') V(a,b) V(c,d)
V(a,OUT) V(c,OUT)

.end

```

 


Fig. 37.2-2 The results of Experiment 37.2-2

Experiment 37.2-3 V1 Decreased from 3V to 2V

In this experiment, V1 is decreased from 3V to 2V. The program is in Table

37.3-3 and the results are in Fig. 37.3-3.

Table 37.3-3 The program for Experiment 37.3-3

```
amplifier
.protect
.lib "C:\model\tsmc\MIXED035\mm0355v.l" TT
.unprotect
.op
.options nomod post

V1 V1 0 2v
V2 V2 0 5v
V1p V1p 0 -2v
V2p V2p 0 -5v

R1 V2 a 5K
R2 V2p c 5K

M1 b a OUT V2p M2N6802 W=2u L=2u
M2 V2 a b V2p M2N6802 W=4u L=2u
M1p d c OUT V2 M2N6804 W=2u L=2u
M2p V2p c d V2 M2N6804 W=4u L=2u

MD1 V1 V1 b V2p M2N6802 W=4u L=2u
MD2 V1p V1p d V2 M2N6804 W=4u L=2u
MD3 a a IN V2p M2N6802 W=2u L=2u
MD4 c c IN V2 M2N6804 W=2u L=2u

RL OUT 0 50

.model M2N6802 NMOS(Level=3 Gamma=0 Delta=0 Eta=0 Theta=0 Kappa=0
Vmax=0 Xj=0
+ Tox=100n Uo=600 Phi=.6 Rs=.1084 Kp=20.88 Vto=2 NSUB=1E15
+ Rd=1.163 Cbd=732p Pb=.8 Mj=.5 Fc=.5 Cgso=1.725n
+ Cgdo=136.7p Is=1.823p N=1 Tt=2060n)

.model M2N6804 PMOS(Level=3 Gamma=0 Delta=0 Eta=0 Theta=0 Kappa=0
Vmax=0 Xj=0
```

```

+      Tox=100n Uo=300 Phi=.6 Rs=.153 Kp=10.46 Vto=-2 NSUB=1E15
+      Rd=66.52m  Cbd=1.281n Pb=.8 Mj=.5 Fc=.5 Cgso=1.798n
+      Cgdo=134.9p  Is=5.477p N=3 Tt=295n)

Vin IN  0  sin(0V 1.5V 3K)

.tran 0.1us 0.6ms
.probe TRAN I(M1) I(M2) I(M1p) I(M2p) power=PAR('V(OUT)*I(RL)') V(a,b)

.end

```

 


Fig. 37.3-3 The results of Experiment 37.3-3

From Fig. 37.3-3, we can see that when V_{in} is larger than 0, M2 conducts. This shows that the circuit does not behave as a Class G power amplifier. Note that $V_1=2V=V_{th}$. Therefore, $V_1-V_{th}=2-2=0$. According to Equation (37-7), in this case, M2 will conduct when V_{in} is larger than 0. Thus the amplifier is not a Class G power amplifier any more.

Experiment 37.2-4 Increasing V_{in} Amplitude from 1.5V to 4V.

In this experiment, the amplitude of V_{in} is increased from 1.5V to 4V. The program is in Table 37.2-4 and the results are in Fig. 37.3-4.

Table 37.2-4 The program for Experiment 37.2-4

```

amplifier

```

```

.protect
.lib "C:\model\tsmc\MIXED035\mm0355v.l" TT
.unprotect
.op
.options nomod post

V1 V1 0 3v
V2 V2 0 5v
V1p V1p 0 -3v
V2p V2p 0 -5v

R1 V2 a 5K
R2 V2p c 5K

M1 b a OUT V2p M2N6802 W=2u L=2u
M2 V2 a b V2p M2N6802 W=4u L=2u
M1p d c OUT V2 M2N6804 W=2u L=2u
M2p V2p c d V2 M2N6804 W=4u L=2u

MD1 V1 V1 b V2p M2N6802 W=4u L=2u
MD2 V1p V1p d V2 M2N6804 W=4u L=2u
MD3 a a IN V2p M2N6802 W=2u L=2u
MD4 c c IN V2 M2N6804 W=2u L=2u

RL OUT 0 50

.model M2N6802 NMOS(Level=3 Gamma=0 Delta=0 Eta=0 Theta=0 Kappa=0
Vmax=0 Xj=0
+ Tox=100n Uo=600 Phi=.6 Rs=.1084 Kp=20.88 Vto=2 NSUB=1E15
+ Rd=1.163 Cbd=732p Pb=.8 Mj=.5 Fc=.5 Cgso=1.725n
+ Cgdo=136.7p Is=1.823p N=1 Tt=2060n)

.model M2N6804 PMOS(Level=3 Gamma=0 Delta=0 Eta=0 Theta=0 Kappa=0
Vmax=0 Xj=0
+ Tox=100n Uo=300 Phi=.6 Rs=.153 Kp=10.46 Vto=-2 NSUB=1E15
+ Rd=66.52m Cbd=1.281n Pb=.8 Mj=.5 Fc=.5 Cgso=1.798n
+ Cgdo=134.9p Is=5.477p N=3 Tt=295n)

```

```

Vin IN 0 sin(0V 4V 3K)

.tran 0.1us 0.6ms
.probe TRAN I(M1) I(M2) I(M1p) I(M2p) power=PAR('V(OUT)*I(RL)') V(a,b)

.end

```

 


Fig. 37.2-4 The results of Experiment 37.2-4

From Fig. 37.2-4, we can see that the circuit does not work because V_a is now equal to $V_{in} + V_{th} = 4 + 2 = 6V$ which is larger than V_2 . M2 becomes saturated.

Experiment 37.2-5 Increasing V_{in} Amplitude from 1.5V to 3V

In this experiment, we increased the V_{in} amplitude from 1.5V to 3V. The program is in Table 37.2-5 and the results are in Fig. 37.2-5.

Table 37.2-5 The program for Experiment 37.2-5

```

amplifier
.protect
.lib "C:\model\tsmc\MIXED035\mm0355v.l" TT
.unprotect
.op
.options nomod post

V1 V1 0 3v

```



```

V2 V2 0 5v
V1p V1p 0 -3v
V2p V2p 0 -5v

R1 V2 a 5K
R2 V2p c 5K

M1 b a OUT V2p M2N6802 W=2u L=2u
M2 V2 a b V2p M2N6802 W=4u L=2u
M1p d c OUT V2 M2N6804 W=2u L=2u
M2p V2p c d V2 M2N6804 W=4u L=2u

MD1 V1 V1 b V2p M2N6802 W=4u L=2u
MD2 V1p V1p d V2 M2N6804 W=4u L=2u
MD3 a a IN V2p M2N6802 W=2u L=2u
MD4 c c IN V2 M2N6804 W=2u L=2u

RL OUT 0 50

.model M2N6802 NMOS(Level=3 Gamma=0 Delta=0 Eta=0 Theta=0 Kappa=0
Vmax=0 Xj=0
+ Tox=100n Uo=600 Phi=.6 Rs=.1084 Kp=20.88 Vto=2 NSUB=1E15
+ Rd=1.163 Cbd=732p Pb=.8 Mj=.5 Fc=.5 Cgso=1.725n
+ Cgdo=136.7p Is=1.823p N=1 Tt=2060n)

.model M2N6804 PMOS(Level=3 Gamma=0 Delta=0 Eta=0 Theta=0 Kappa=0
Vmax=0 Xj=0
+ Tox=100n Uo=300 Phi=.6 Rs=.153 Kp=10.46 Vto=-2 NSUB=1E15
+ Rd=66.52m Cbd=1.281n Pb=.8 Mj=.5 Fc=.5 Cgso=1.798n
+ Cgdo=134.9p Is=5.477p N=3 Tt=295n)

Vin IN 0 sin(0V 3V 3K)

.tran 0.1us 0.6ms
.probe TRAN I(M1) I(M2) I(M1p) I(M2p) power=PAR('V(OUT)*I(RL)') V(a,b)

.end

```

 


Fig. 37.2-5 The results of Experiment 37.2-5

We can see that the circuit works in this case. Note that $V_a = V_{in} + V_{th} = 3 + 2 = 5V$ which is exactly equal to V_2 . In the next experiment, we will show that the amplitude of V_{in} cannot be larger than $3V$.

Experiment 37.2-6 V_{in} Amplitude Equal to $3.3V$

In this experiment, V_{in} amplitude is $3.3V$. The program is in Table 37.2-6 and the results are in Fig. 37.2-6. Since $V_a = V_{in} + V_{th} = 3.3 + 2 = 5.3V$ which is larger than V_2 , the circuit does not work.

Table 37.2-6 The program for Experiment 37.2-6

```

amplifier
.protect
.lib "C:\model\tsmc\MIXED035\mm0355v.l" TT
.unprotect
.op
.options nomod post

V1 V1 0 3v
V2 V2 0 5v
V1p V1p 0 -3v
V2p V2p 0 -5v

```

```

R1 V2 a 5K
R2 V2p c 5K

M1 b a OUT V2p M2N6802 W=2u L=2u
M2 V2 a b V2p M2N6802 W=4u L=2u
M1p d c OUT V2 M2N6804 W=2u L=2u
M2p V2p c d V2 M2N6804 W=4u L=2u

MD1 V1 V1 b V2p M2N6802 W=4u L=2u
MD2 V1p V1p d V2 M2N6804 W=4u L=2u
MD3 a a IN V2p M2N6802 W=2u L=2u
MD4 c c IN V2 M2N6804 W=2u L=2u

RL OUT 0 50

.model M2N6802 NMOS(Level=3 Gamma=0 Delta=0 Eta=0 Theta=0 Kappa=0
Vmax=0 Xj=0
+ Tox=100n Uo=600 Phi=.6 Rs=.1084 Kp=20.88 Vto=2 NSUB=1E15
+ Rd=1.163 Cbd=732p Pb=.8 Mj=.5 Fc=.5 Cgso=1.725n
+ Cgdo=136.7p Is=1.823p N=1 Tt=2060n)

.model M2N6804 PMOS(Level=3 Gamma=0 Delta=0 Eta=0 Theta=0 Kappa=0
Vmax=0 Xj=0
+ Tox=100n Uo=300 Phi=.6 Rs=.153 Kp=10.46 Vto=-2 NSUB=1E15
+ Rd=66.52m Cbd=1.281n Pb=.8 Mj=.5 Fc=.5 Cgso=1.798n
+ Cgdo=134.9p Is=5.477p N=3 Tt=295n)

Vin IN 0 sin(0V 3.3V 3K)

.tran 0.1us 0.6ms
.probe TRAN I(M1) I(M2) I(M1p) I(M2p) power=PAR('V(OUT)*I(RL)') V(a,b)

.end

```

 


Fig. 37.2-6 The results of Experiment 37.2-6